

平面顯示技術導論 HW #2

B02901178 江誠敏

June 6, 2016

1. An equivalent circuit of a single LCD pixel is shown below. The transistor will be replaced by a 50Ω resistor which is connected between V_s and V_d . Assuming $C_{st} = 3\text{ pF}$, and $C_{lc} = 5\text{ pF}$, a step function V_G is applied at $t = 0$ to turn on the TFT, $V_D = 0$ (at $t < 0$), $V_S = 5\text{ V}$.

- (a) Please calculate how long it takes to charge up C_{lc} from 0 V to 90% of V_s (i.e. 4.5 V).

Ans: First we calculate the time constant $\tau = R(C_{lc} + C_{st}) = 0.4\text{ ns}$.

$$e^{-t/\tau} = 1 - 0.9 \quad \Rightarrow \quad t = \tau \log 10 \quad \Rightarrow \quad t \approx 0.92\text{ ns}$$

- (b) Please calculate how long it takes to charge up C_{lc} from 0 V to 4.5 V if V_s becomes 9 V .

Ans: The time constant remains the same, but now 4.5 V is only 50% of 9 V .

$$e^{-t/\tau} = 1 - 0.5 \quad \Rightarrow \quad t = \tau \log 2 \quad \Rightarrow \quad t \approx 0.277\text{ ns}$$

- (c) Please comment on the overdrive technology.

Ans: The overdrive technology would give better respond speed, since its charging time is shorter.

2. Questions:

- (a) What is the duration (time), T_3 , of the scan line 110? And what is $(t_2 - t_1)$ when the data line is enabled?

Ans: If 320×120 means that there are 320 scan lines, then

$$T_3 = 1\text{ s}/30/320 \approx 104.2\text{ }\mu\text{s},$$

Else

$$T_3 = 1\text{ s}/30/120 \approx 277.8\text{ }\mu\text{s}.$$

No matter what, we have

$$(t_2 - t_1) = 1 \text{ s} / 30 / 120 / 320 \approx 0.868 \mu\text{s}$$

(b) What is the maximum capacitance of capacitor 104?

Ans: Let $\Delta t = (t_2 - t_1)/2$, $\tau = RC$ where $R = 10 \Omega$.

$$\begin{aligned} e^{-\Delta t/\tau} &\leq 1 - 0.8 \implies \frac{\Delta t}{\tau} \geq \log 5 \implies RC = \tau \leq \frac{\Delta t}{\log 5} \\ \implies C &\leq \frac{\Delta t}{R \log 5} = \frac{t_2 - t_1}{2R \log 5} \approx 27.0 \text{ nF} \end{aligned}$$

(c) Assuming the first OLED selected in the columns, after the data line is disable, the circuit is in the discharge process. Can the fully-on period of the OLED last the entire scan line period (T_3)?

Ans: No, from the previous question we knew that

$$\tau \leq \frac{\Delta t}{\log 5}$$

Let V^* be the voltage of capacitor 104 just after the data line is disabled, and we know that $V^* \leq V_{\text{data}}$. Let t^* be the time needed for the voltage to drop to $0.8V_{\text{data}}$, which is greater than $0.8V^*$, then

$$t^* \leq \tau(-\log 0.8) = \frac{\log 5/4}{\log 5} \Delta t \approx 0.14 \Delta t,$$

Which is much smaller than $2\Delta t = t_2 - t_1$, and not to mention T_3 .

(d) Please plot (hand draw is OK) I_{OLED} vs. time once V_{data} is enabled.

We knew that $V_{104} = V_{\text{data}}(1 - e^{-t/\tau})$ from the previous problems. And we assume that $I_{\text{OLED}} \propto V_{104}^2$ (Since $I \propto V^2$ in MOS).

